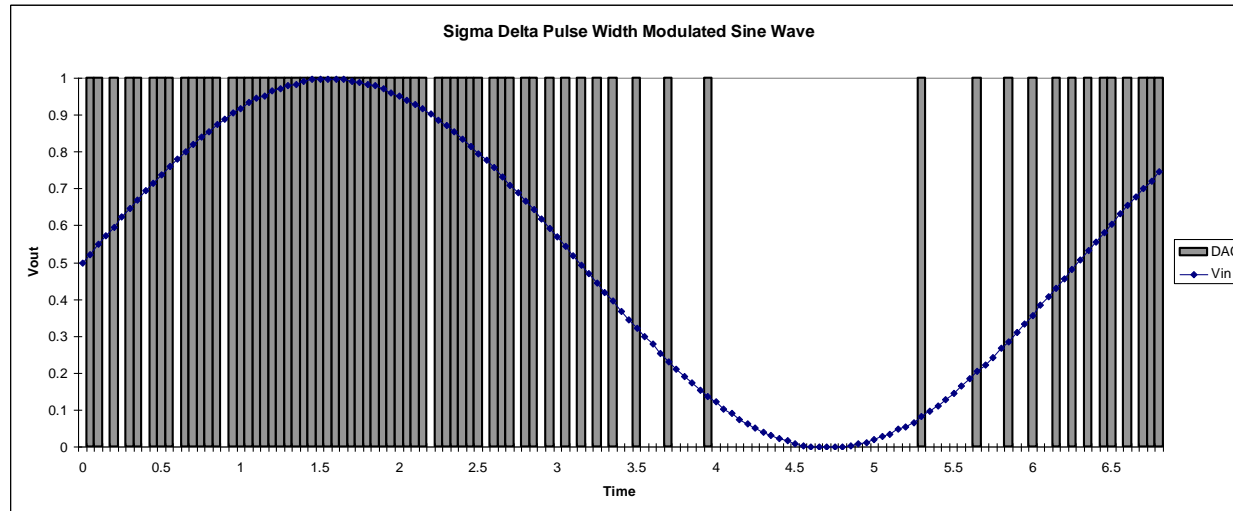


# Pulse Width Modulation & FPGA




BFY


AAPT Philadelphia 2012  
Kurt Wick (wick@umn.edu)  
University of Minnesota
 
# PWM Theory

$$\langle V_{out} \rangle = \frac{\tau_{on}}{\tau_{swc}} V_{on}$$



# PWM Circuit Components

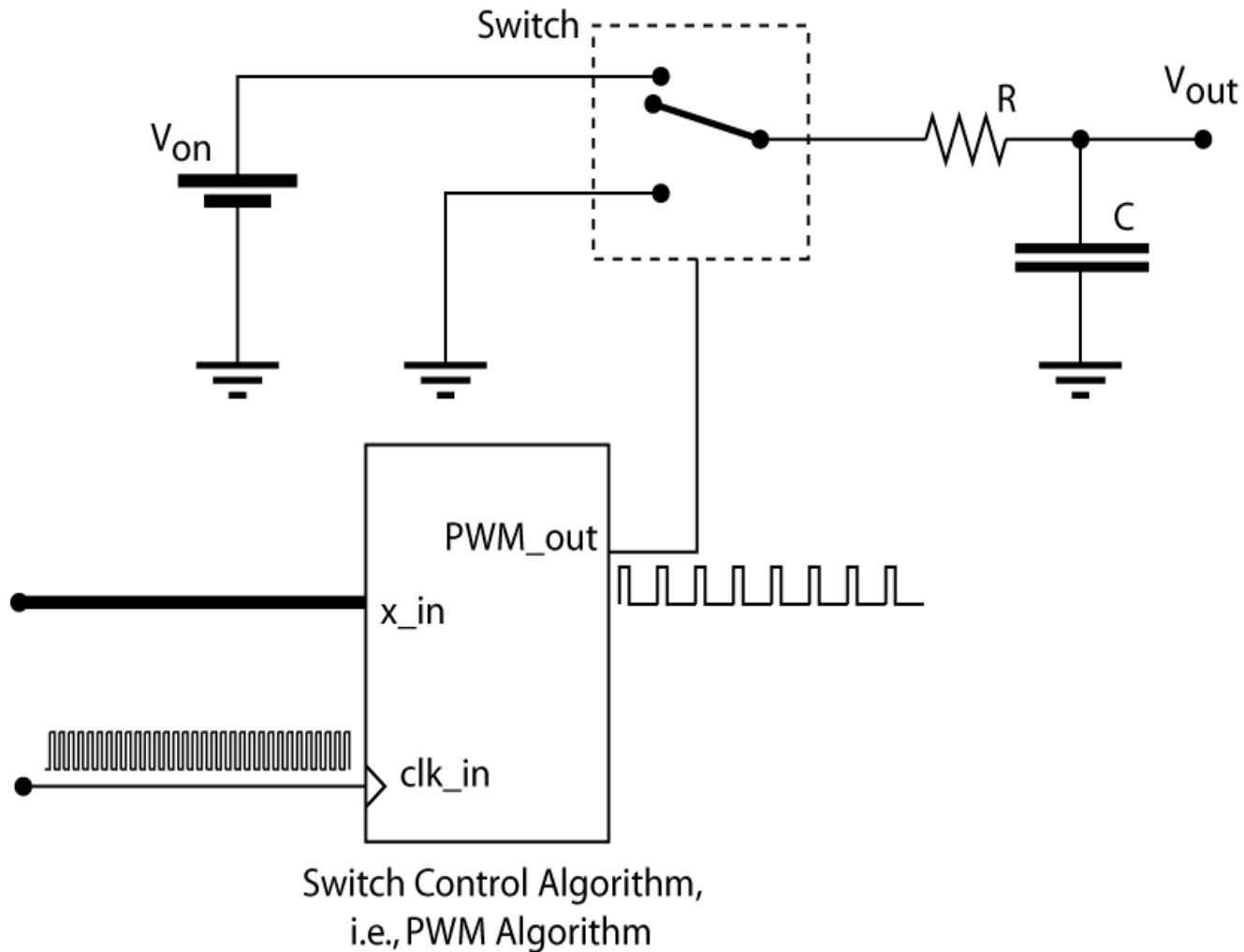

# Simple PWM Control Algorithm

- *An  $n$ -bit counter continuously increments from 0 to its maximum value, i.e.,  $2^n-1$  and then repeats the cycle.*
- *Range of input value  $x_{in}$ :  $0 \leq x_{in} \leq 2^n-1$*


**if ( counter < x\_in )**

**PWM\_out <= 1;**

**else**

**PWM\_out <= 0;**

**counter <= counter+1;**

 

Switch Control Algorithm,  
i.e., PWM Algorithm

# Verilog Implementation of Simple 8 Bit PWM Algorithm


```
module SimplePWM(clk_in, x_in, PWM_out);

    input clk_in;    //clock for counter
    input [7:0] x_in;    //control value that
                        //defines pulse width
    output reg PWM_out = 1;    //PWM signal out

    reg [7:0] counter = 0;

    always@ (posedge clk_in )begin
        if ( counter < x_in )
            PWM_out <= 1;
        else
            PWM_out <= 0;
        counter <= counter+1;
    end

endmodule
```

 

Switch Control Algorithm,  
i.e., PWM Algorithm

# A2D Key Concepts:

## Resolution / Sensitivity

- Resolution of an n-bit PWM A2D is:  $V_{on} / 2^n$
- (Hypothetical) Resolution for our BASYS board PWM A2D with  $V_{on} = 5$  Volts would be:

bits	Resolution (Volts)
8	1.9E-02
16	7.6E-05
32	1.2E-09
64	2.7E-19

# A2D Key Concepts:





## Conversion Time

- It takes at least one complete counter cycle to average  $V_{out}$ . For a counter running at  $f_o$ , this corresponds to:  $2^n/f_o$
- (Optimal) Conversion Time for our BASYS board PWM A2D with  $f_o = 25$  MHz:

Bits	Resolution (Volts)	Conversion Time
8	1.9E-02	10.2 usec
16	7.6E-05	2.6 msec
32	1.2E-09	2.8 min
64	2.7E-19	23000 years

    
# Sigma Delta Concepts

Though  $V_{\text{out}}(t)$  is different in each of these timing diagrams,  $\langle V_{\text{out}} \rangle$  remains identical.






# Sigma Delta PWM Algorithm

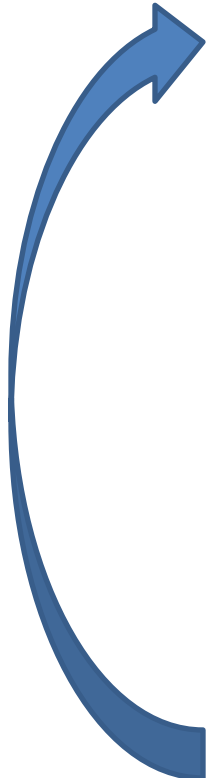

 
```
if ( Sigma >= Delta )
{
    Sigma = (Sigma - Delta) + x_in;
    Out = 1;
}
else
{
    Sigma = Sigma + x_in;
    Out = 0;
}
```



Switch Control Algorithm,  
i.e., PWM Algorithm

# PWM Application: Music Player

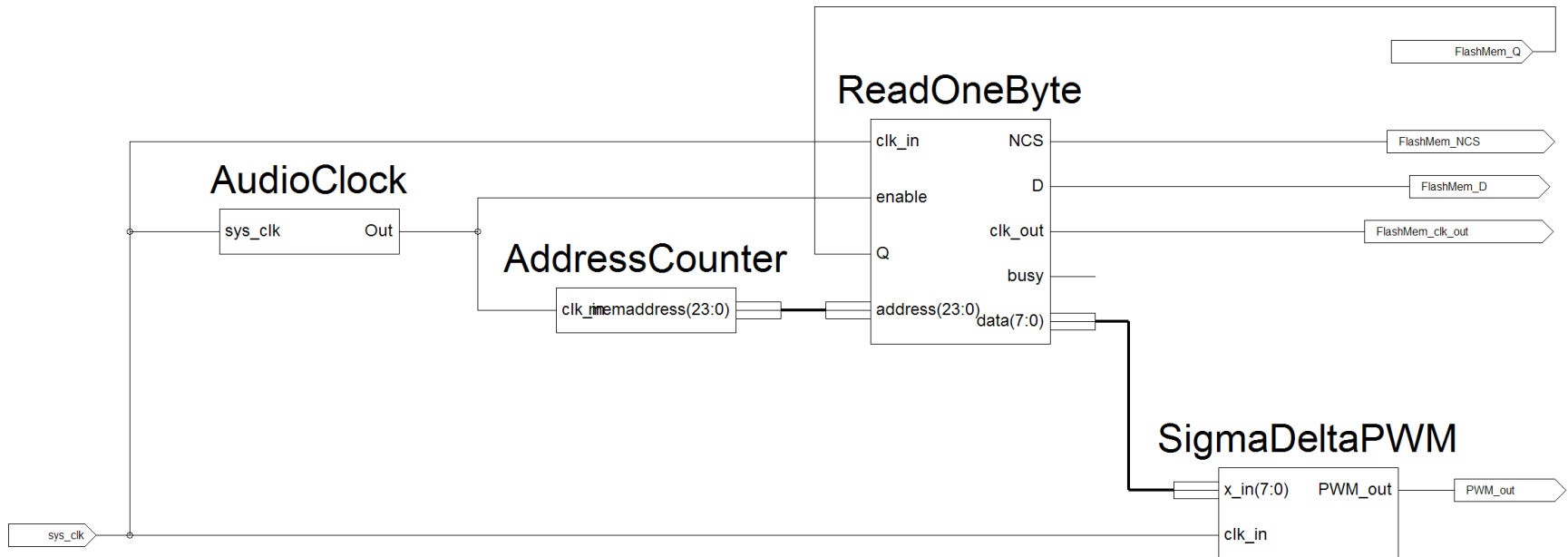

# Conclusions about PWM

- Pulse Width Modulation can be used to create an analog signal from a digital signal.
- Allows the reduction of a DC signal while being much more energy efficient than, for example, a passive voltage divider.
- Sigma Delta algorithm can also be used for voltage to frequency conversion.

# Educational Goals

- The PWM exercises expose students to basic digital concepts such as clocks and counters.
- They are easily implemented with an FPGA and thereby exposes students with this ubiquitous electronic component.
- Familiarizes them with digital-to-analog converters and the basic concepts of resolution and conversion time.
- The exercise can be extended by turning it into an analog-to-digital converter using successive approximation and a state machine.